



**Faculty of Engineering & Technology**  
**Electrical & Computer Engineering Department**

## **ENEE2360 Project**

**Prepared by: Rana Musa    1210007**

**Malak Alaraj**

**Dr. Nasser Ismail**

**Section 3**

## Contents



<b>Abstract.....</b>	<b>3</b>
<b>Part1(Practical).....</b>	<b>4</b>
a) Construct the circuit to verify its function. ....	4
b) Set $R_s$ to $22K\Omega$ , determine the value of $V_{o1}$ , $V_{o2}$ , $V_{o3}$ , $V(+)$ and $V(-)$ of each OpAmp. Also indicate the status of each LED.....	5
c) Repeat step(b) for $R_s = 25K\Omega$ and $R_s = 20K$ .....	6
d) Determine the $T$ upper limit and the $T$ lower limit .....	8
<b>Part2 Simulation circuits and results .....</b>	<b>10</b>
b) Simulate the circuit for $R_s = 22K, 25K$ , and $20K$ .....	10
c) Replacing the shaded part by a VPWL Voltage source as shown in Fig.(2) , plot $V_{o1}(t)$ , $V_{o2}(t)$ , and $V_{o3}(t)$ . ....	13
d) Estimate the upper limit and the lower limit temperatures from $V_{o2}$ and $V_{o3}(t)$ plots. ....	14
f) Calculate by hand the upper threshold and the lower threshold temperature.....	16
g) Comparison of simulation results to hand calculation:.....	20
<b>conclusion .....</b>	<b>21</b>

## Abstract

Using a Thermistor and two LEDs, the circuit's goal is to track and signal temperature changes. Based on the temperature range, the circuit is designed to give visual feedback. The temperature sensor is a 20K Thermistor with a nominal resistance at 25°C. To show temperature conditions, the circuit uses two LEDs: a Red LED (D1) and a Green LED (D2).

## Part1(Practical)

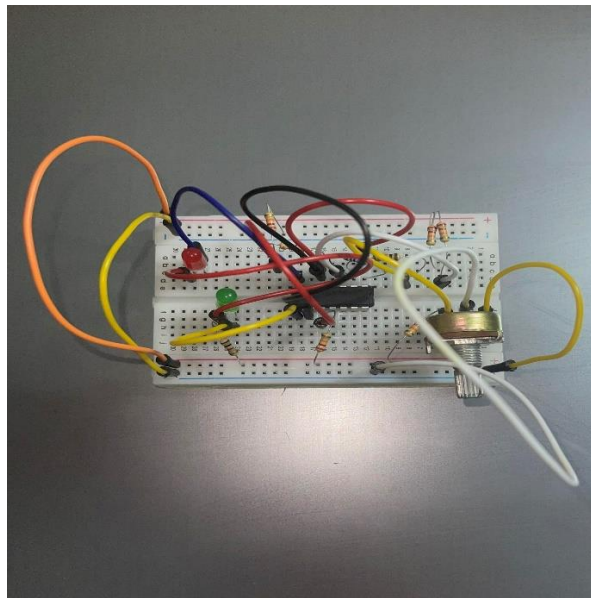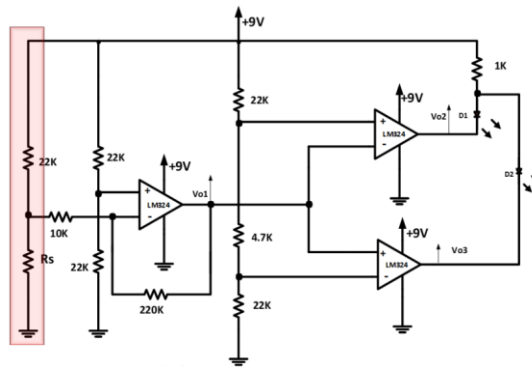a) Construct the circuit to verify its function.



This circuit consists of three operational amplifiers. The first one is inverting subtractor such that the result will be the difference between it both terminals. It is also consisted of 2 others amplifiers which are comparators, if  $V_d > 0$  the output will be  $+V_{sat}$ , if  $V_d < 0$  the output will be  $-V_{sat}$ . And this what control the light of green and red leds.

b) Set  $R_s$  to  $22K\Omega$ , determine the value of  $V_{o1}, V_{o2}, V_{o3}, V(+)$  and  $V(-)$  of each OpAmp. Also indicate the status of each LED

part 1: practical:

set  $R_s$  to  $22K$

OpAmp 4

$V_a = \frac{22k}{22k+22} \times 9V = 4.5 \text{ volts}$

$V(+)= \frac{22k}{22k+22k} \times 9V = 4.5 \text{ volts}$

$V(-) = V(+)= 4.5 \text{ volts}$

nodal at  $V(-)$

$$\frac{V(-)-V_a}{10k} + \frac{V(-)-V_o}{220k} = 0$$

$$\frac{4.5-4.5}{10k} + \frac{4.5-V_o}{220k} = 0$$

$V_{o1} = 4.5 \text{ Volts}$

$V(+)= \frac{4.7k+22k}{4.7k+22k+22k} \times 9$

$V(+)= 4.934 \text{ Volts}$


$V(-) = V_{o1} = 4.5 \text{ Volts}$

$V(+)>V(-)$


$V_{o2} = +V_{sat}$

red light on

OpAmp 2

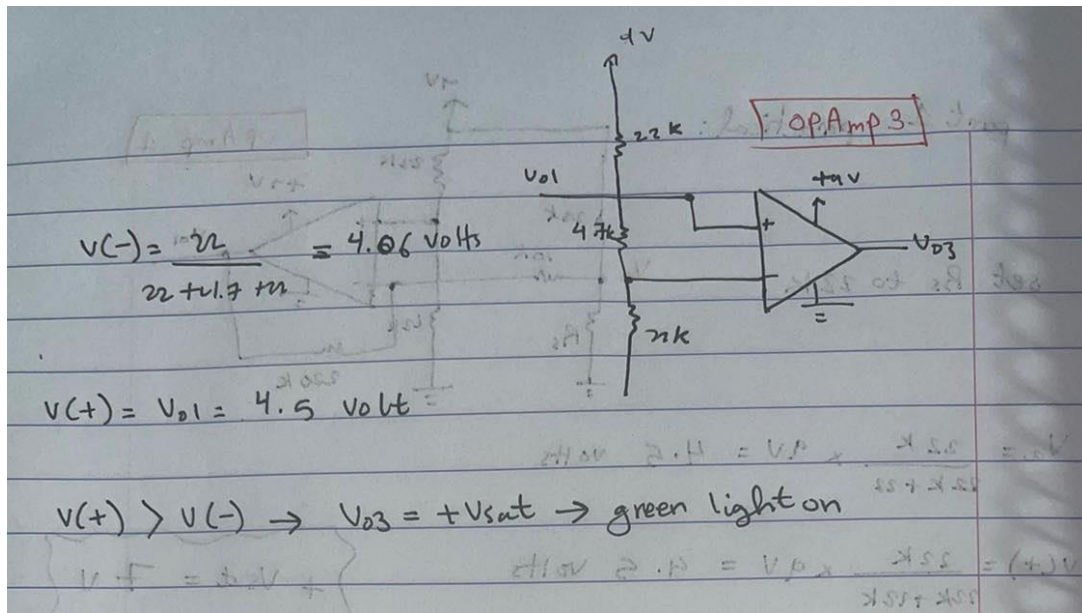

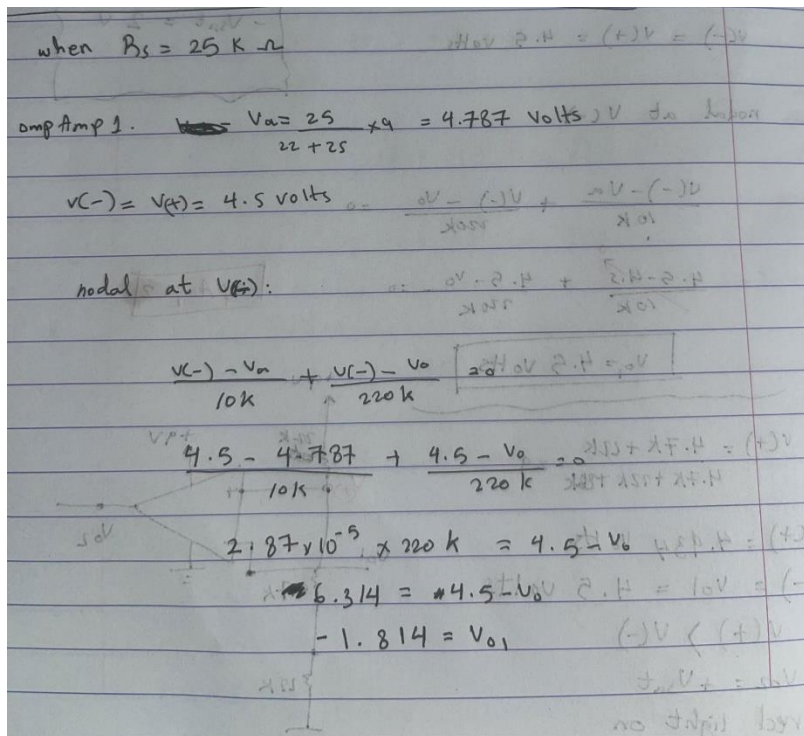c) Repeat step(b) for  $R_s = 25\text{K}\Omega$  and  $R_s = 20\text{K}$





at opamp 2:

$V(-) > V(+)$   $\Rightarrow V_{O2} = +V_{sat}$  red light on  $(-V < 0V)$

$$\therefore V(+)=4.934 \text{ volts}$$

$$V(-)=V_{O1}=-1.814 \text{ volts}$$

at opamp 3:

$$V(-)=4.06 \text{ volts}$$

$$V(+)= -1.814 \text{ volts}$$

$V(-) > V(+)$   $\Rightarrow V_{O3} = -V_{sat}$  green light is off

when  $R_5 = 20k\Omega$   $\Rightarrow$   $V_{O3} = -V_{sat}$   $\Rightarrow$  green light is off

at opamp 1:  $V_a = \frac{20}{20+22} \times 9 = 4.28 \text{ volts}$

$$V(-)=V(+)=4.5 \text{ volts}$$

$$\frac{V(-)-V_a}{10k} + \frac{V(-)-V_o}{220k} = 0$$

$$\frac{4.5-4.28}{10k} + \frac{4.5-V_o}{220k} = 0$$

$$V_{O1} = 9.214 \text{ volts}$$

at opamp 2:  $V(-) > V(+)$   $\therefore V(+)=4.934 \text{ volts}$

$V_{O2} = -V_{sat} \rightarrow$  red light off  $V(-)=V_{O1}=9.214 \text{ volts}$

at opamp 3:

$V(+) > V(-)$  since  $V(+) = 0V = 9.241 \text{ volts}$

$V(-) = 14.06 \text{ Volts}$

$11.0V \text{ } 18.1 = 1.0V = (-)V$

$V_{03} = +V_{sat}$

green led is ON.

d) Determine the T upper limit and the T lower limit

T upper and lower limits when  $R_s = 20k$

which is the critical thermostat resistance

(from calculations)

$T_{upper} = 22.423^\circ C$  this occurs when resistance is  $22200 \Omega$  from data sheet (approximately)

$T_{lower} = 18.477$  (from calculations), this occurs when resistance is between  $27472$  and  $26.037$  from data sheet (approximately).



## Data sheet results



57	13.89	34165
59	15.00	32336
61	16.11	30615
63	17.22	28996
65	18.33	27472
67	19.44	26037
69	20.56	24674
71	21.67	23400
73	22.78	22200
75	23.89	21068
77	25.00	20001

57	13.89	34165
59	15.00	32336
61	16.11	30615
63	17.22	28996
65	18.33	27472
67	19.44	26037
69	20.56	24674
71	21.67	23400
73	22.78	22200
75	23.89	21068
77	25.00	20001



## Part2 Simulation circuits and results

b) Simulate the circuit for  $R_s = 22K, 25K$ , and  $20K$



When  $R_s = 20K$

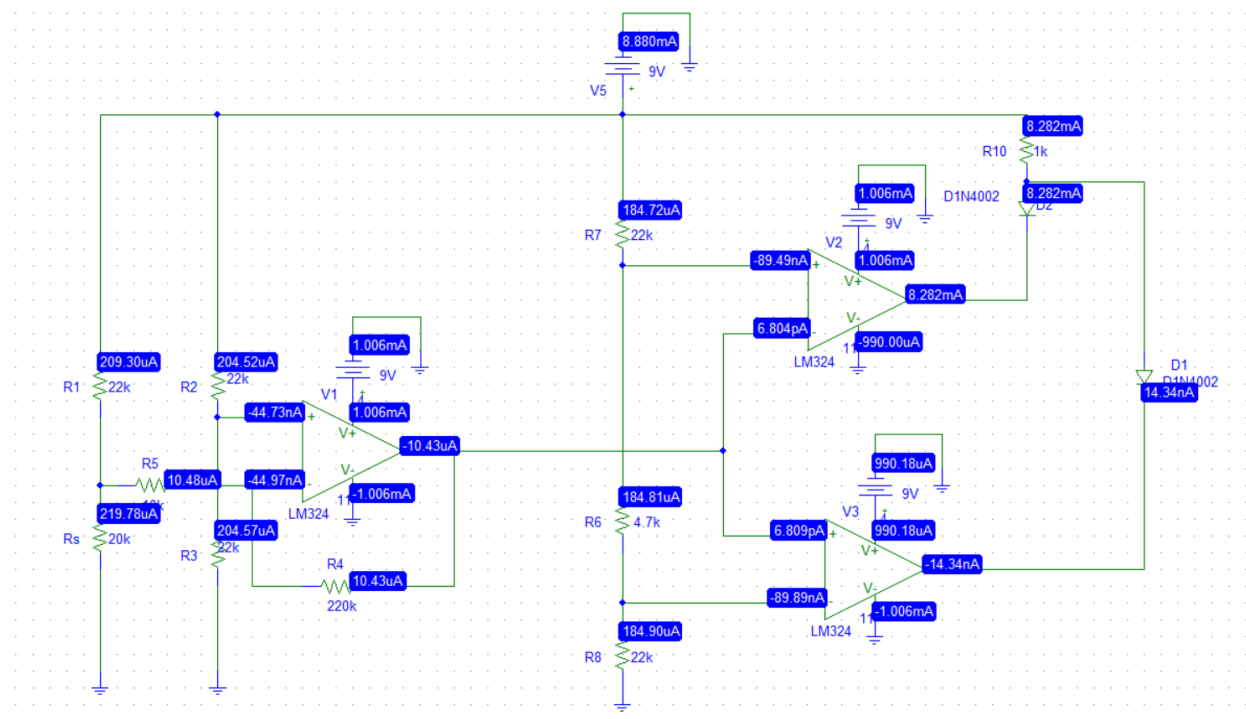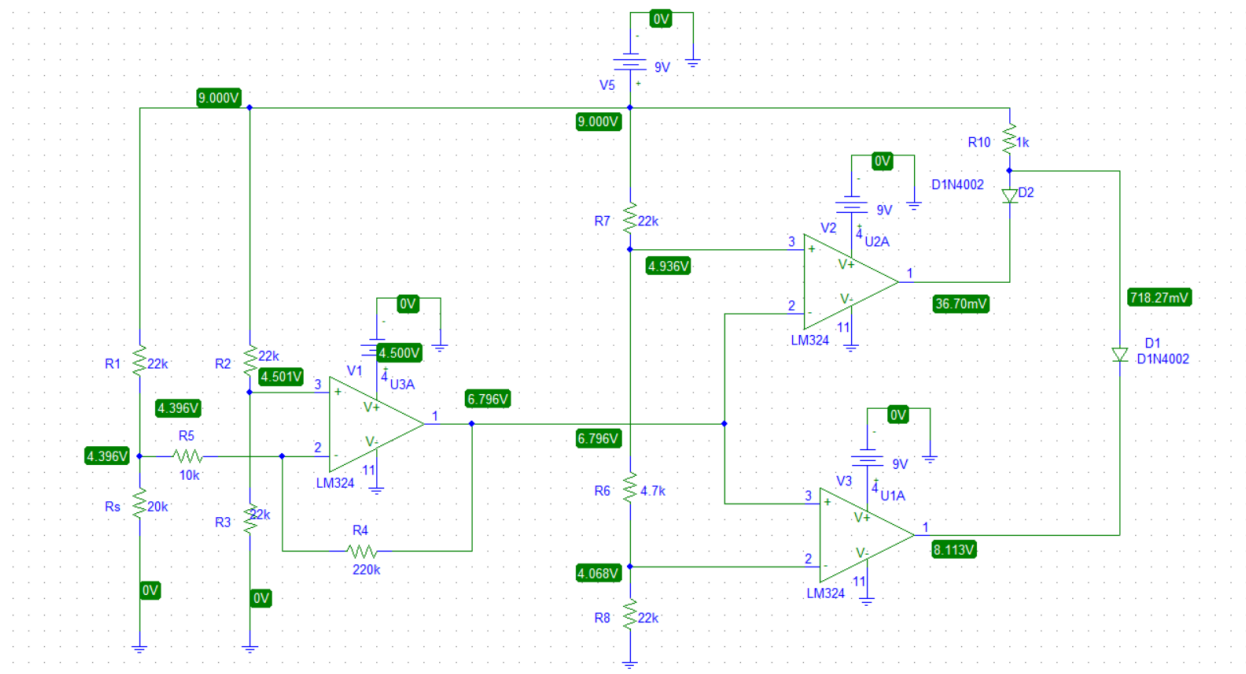

When  $R_s=22k$

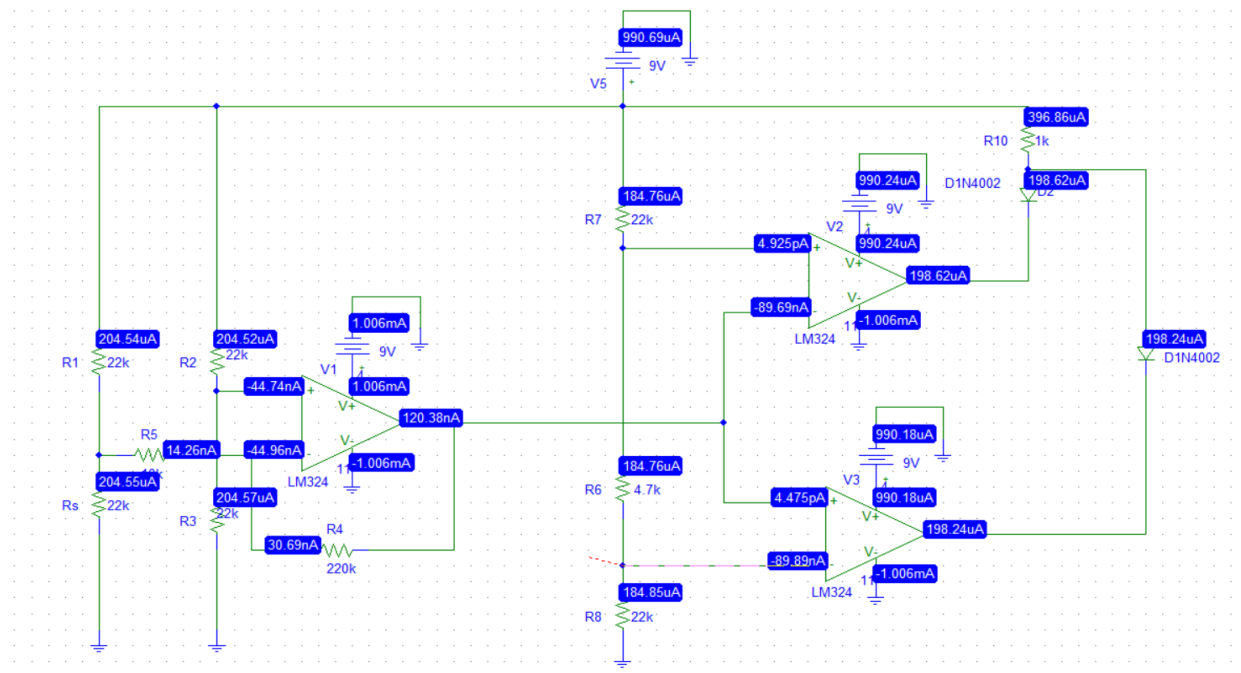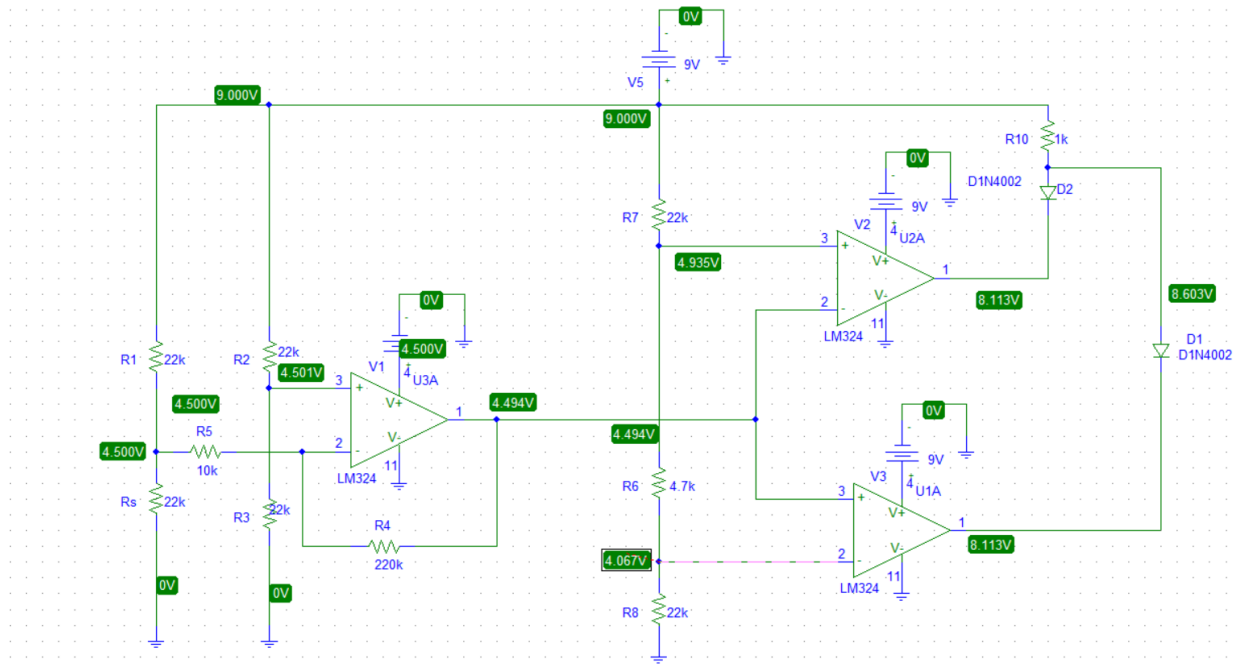

When  $R_s=25k$

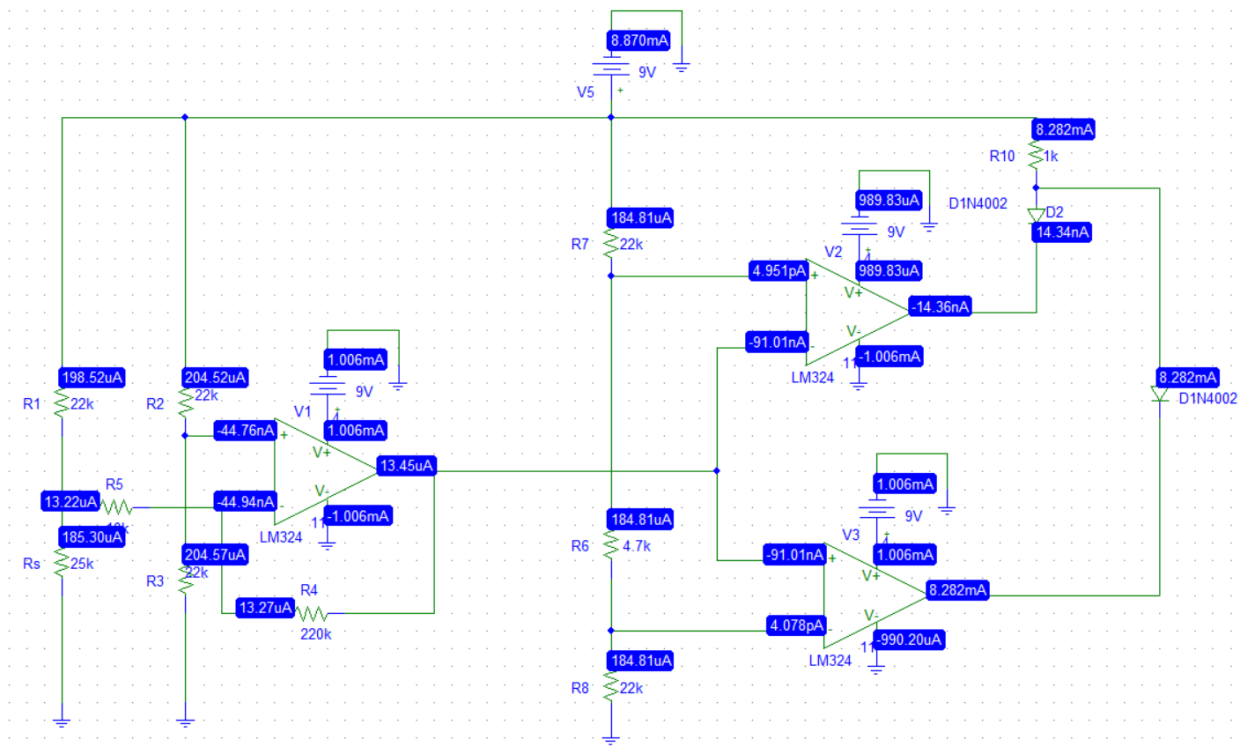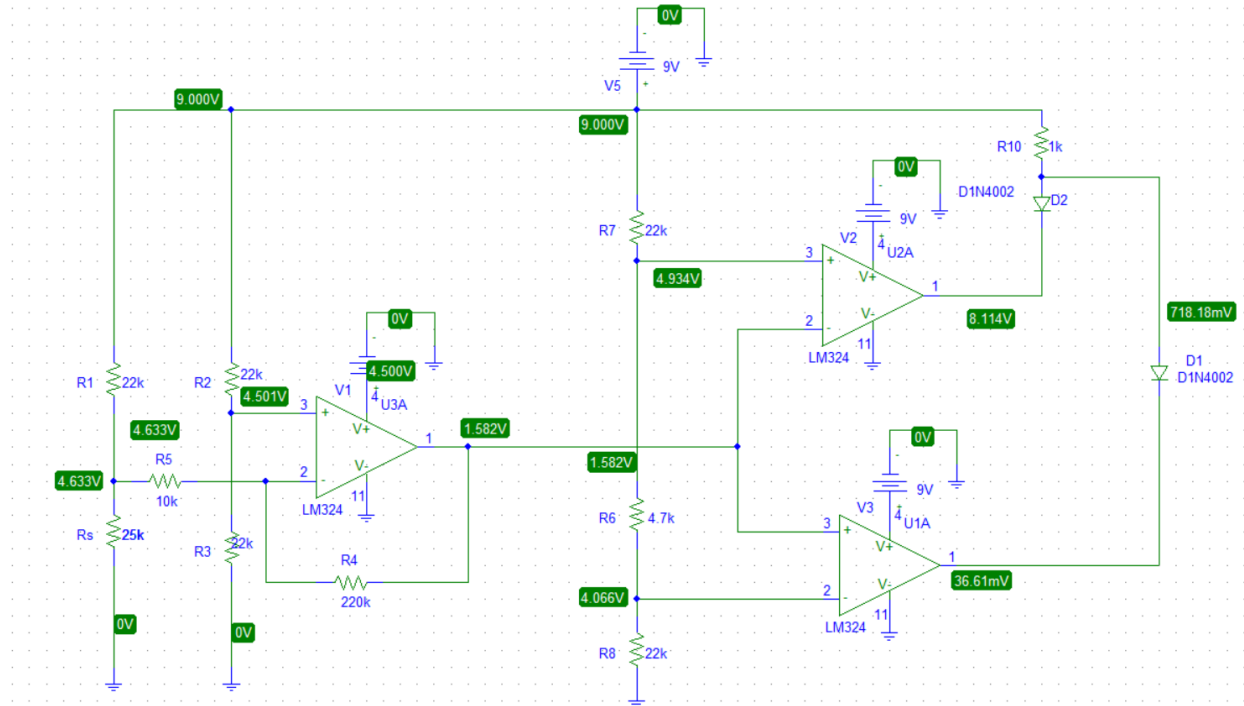

c) Replacing the shaded part by a VPWL Voltage source as shown in Fig.(2) , plot  $V_{o1}(t)$ ,  $V_{o2}(t)$ , and  $V_{o3}(t)$ .

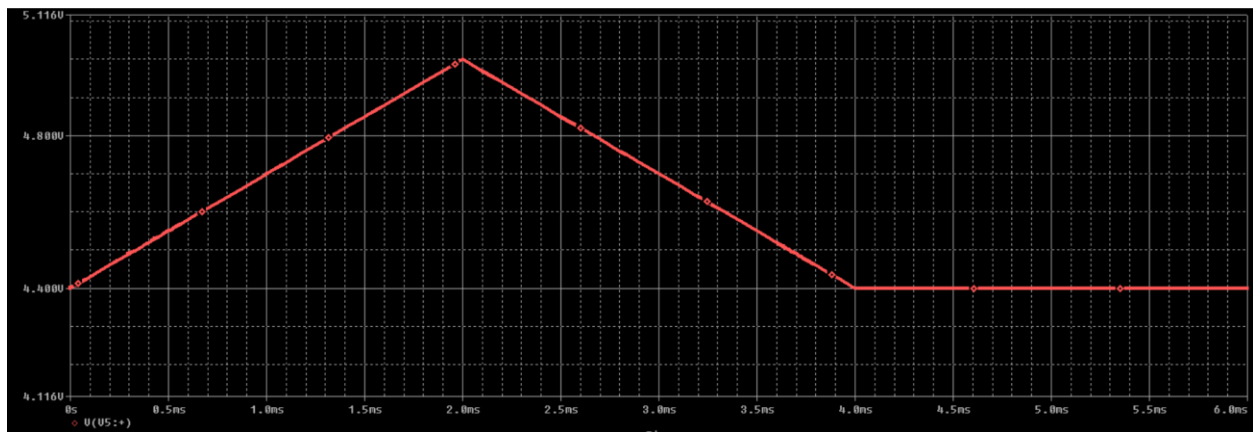


Figure 1: VPWL


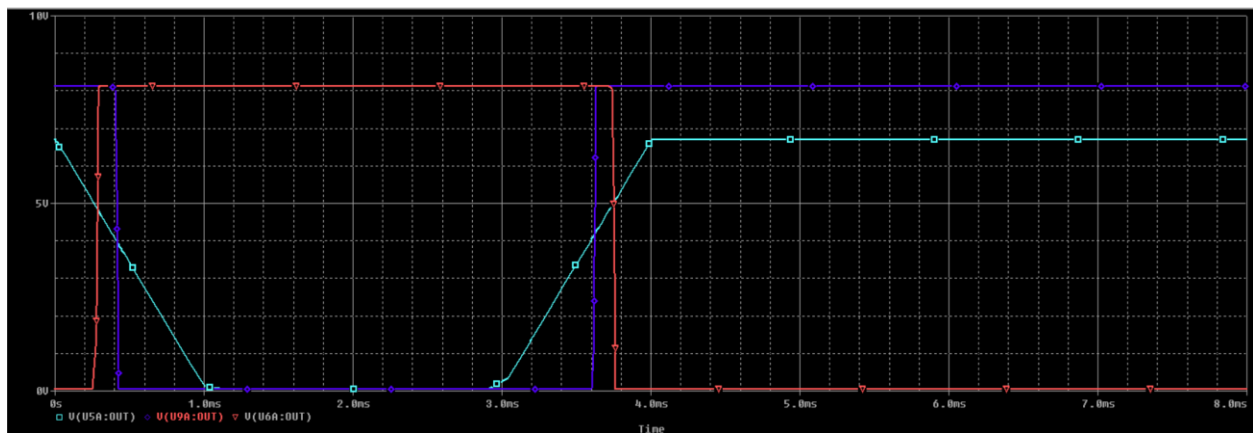


Figure 2:  $V_{o1}$ ,  $V_{o2}$ ,  $V_{o3}$  plots

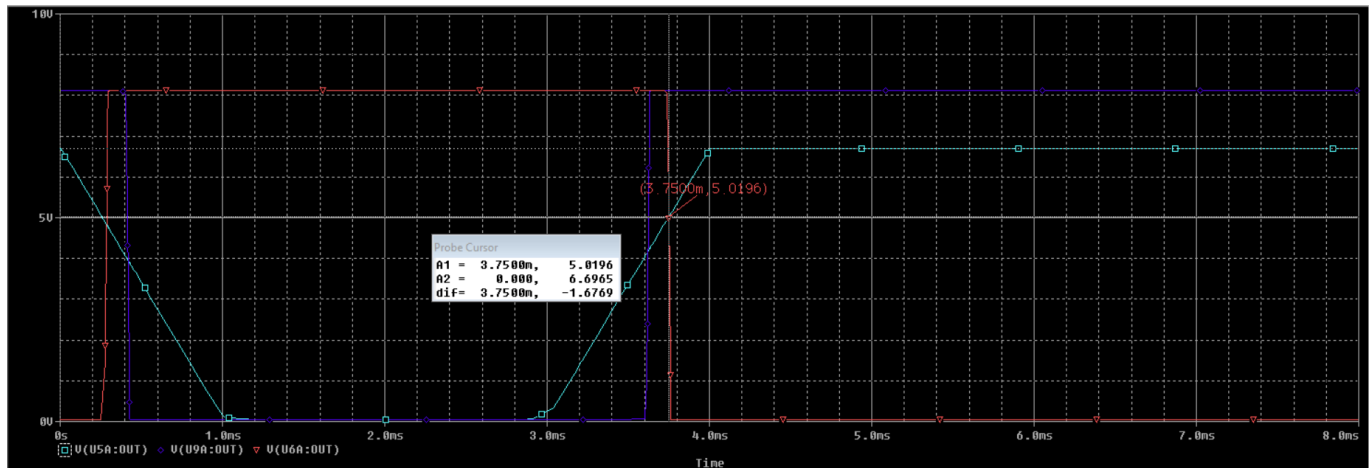


d) Estimate the upper limit and the lower limit temperatures from Vo2 and Vo3(t) plots.

### Upper Threshold



### Lower Threshold

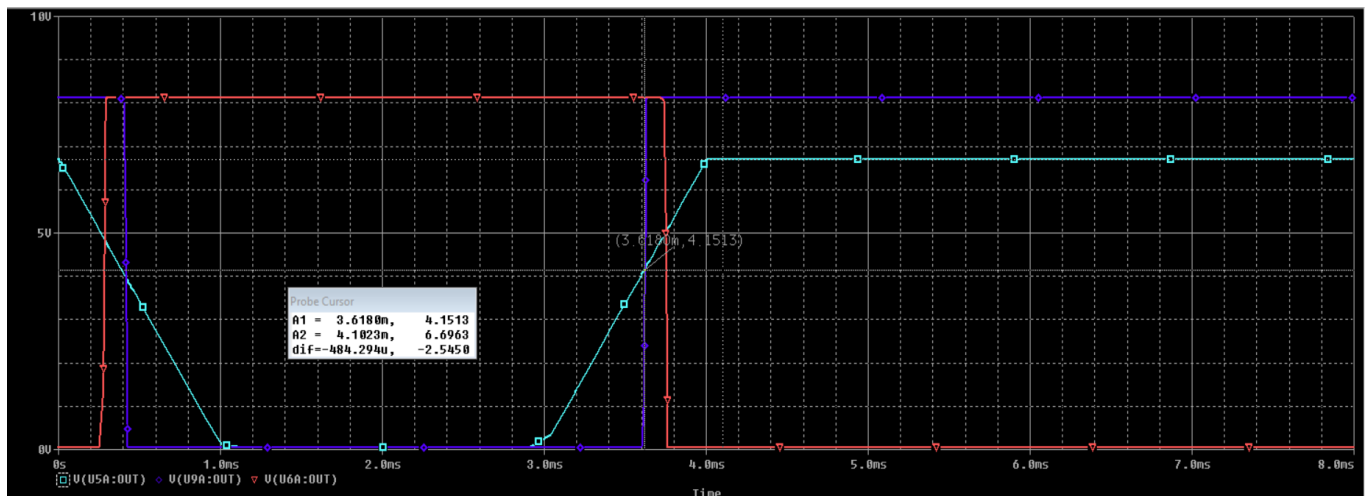

From pspice:

upper threshold = 5.0196 , gain = 22

$$\frac{5.0196}{22} = 0.22816 \text{ V} = 228.163 \text{ mV}$$

1 → 10 mV (from notes)

5 → 228.163

upper temperature = 22.8163°C

---

Lower threshold = 4.1513 volts

$$\frac{4.1513}{22} = 188.645 \text{ mV}$$

1 → 10 mV (from notes)

5 → 188.645

Lower temperature = 18.8645

f) Calculate by hand the upper threshold and the lower threshold temperature

inverting subtractor

at node a:

$$i_f = i_i$$

$$\frac{V_1 - V_o}{R_1} = \frac{V_a - V_o}{R_2}$$

$$V_o = \left( \frac{R_2}{R_1} + 1 \right) V_a - \frac{R_2}{R_1} V_1 \quad (1)$$

at node b:

$$V_b = V_2 \cdot \frac{R_4}{R_3 + R_4} = V_a$$

$$\therefore V_o = \left( \frac{R_2}{R_1} + 1 \right) \left[ \frac{R_4}{R_3 + R_4} \cdot V_2 - \frac{R_2}{R_1} \cdot V_1 \right]$$

$$V_o = \frac{R_2 (1 + R_1/R_2)}{R_1 (1 + R_3/R_4)} \cdot V_2 - \frac{R_2}{R_1} \cdot V_1$$


$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

$$\text{gain} = \frac{R_2}{R_1} = 22$$

$$V(+)=\frac{22K}{22K+22K} \times (9V)$$

$$= \boxed{4.5V}$$
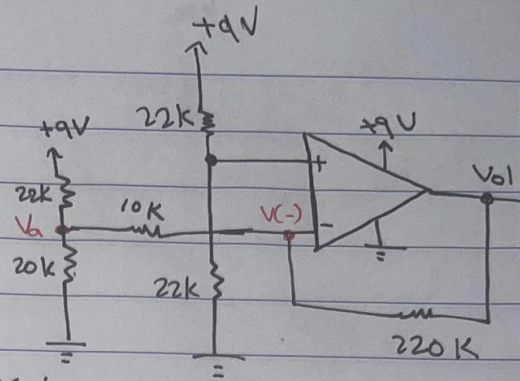
$$V_a = \frac{20K}{22K+20K} (9) = 4.396V$$



nodal at  $V(-)$ :

$$\frac{V(-) - V_a}{10K} + \frac{V(-) - V_{ol}}{220K} = 0$$

$V(-) = V(+)= 4.5$  volts since it is ideal opAmp

$$\Rightarrow \frac{4.5 - 4.396}{10K} + \frac{4.5 - V_{ol}}{220K} = 0$$

$$-1.04 \times 10^{-5} = \frac{4.5 - V_{ol}}{220K}$$

$$\boxed{6.788 \text{ Volts} = V_{ol}}$$




comparator:

$$V_{ref} = \frac{22 + 4.7}{22 + 4.7 + 22} \times 9V$$

$$V(+)=V_{ref} = 4.9342 \text{ Volts}$$

$$V(-)=V_{o1} = 6.788$$

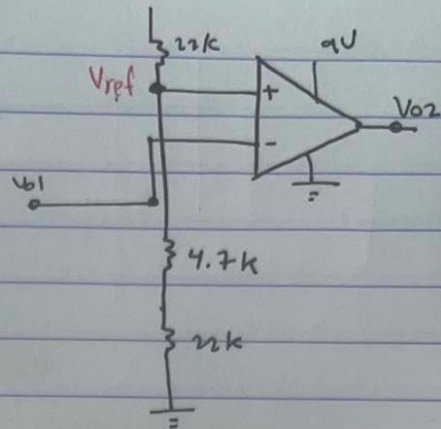


$V_d < 0V$  ;  $V_o = -V_{sat} = 9 - 2 = 7 \text{ volts} \Rightarrow \text{red Led is off}$

$$V_{ref} = \frac{22k}{22k + 22k + 4.7k} \times 9V$$

$$V(-)=V_{ref} = 4.665 \text{ Volts}$$

$$V(+)=V_{o1} = 6.788$$

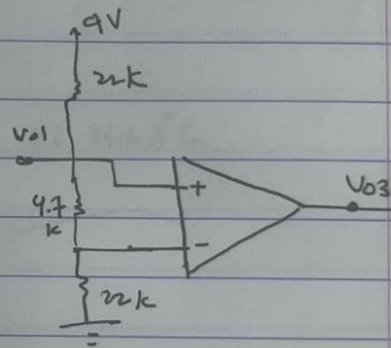

$V_d > 0$  ,  $V_o = +V_{sat} = 9 - 2 = 7 \text{ volts} \Rightarrow \text{green Led is on}$



upper and lower temperatures.

$$\text{gain} = 22$$

$$V_{\text{ref1}} = 4.9342 \text{ volts}$$

$$\frac{4.9342}{22} = 224.2818 \text{ mV}$$

$$1 \rightarrow 10 \text{ mV}$$

$$S \rightarrow 224.2818 \text{ mV}$$

$$U_T = \frac{224.2818}{10} = 22.428^\circ\text{C}$$

$$V_{\text{ref2}} = 4.065 \text{ volts}$$

$$\frac{4.065}{22} = 0.1847 \text{ volts} = 184.77 \text{ mV}$$

$$1 \rightarrow 10 \text{ mV}$$

$$S \rightarrow 184.77 \text{ mV}$$

$$L_T = \frac{184.77}{10} = 18.477^\circ\text{C}$$

g) Comparison of simulation results to hand calculation:

*From result in PSpice:*

- **VUt=5.0196 volts VLt=4.1513 volt**
  - **ut=22.8163C, lt=18.8965C**
- 

*Theoretical:*

- **+Vsat=+vcc-2=9-2=7 volt**
- **-Vsat=-vcc+2=0+2=2 volt**
- **VUt=4.9342 volts, VLt=4.065 volts**
- **Ut=22.428 c ,Lt=18.477 c**

**According to the results, the results are close.**

**The difference due to different reasons such as equations that are used in hand calculations are not fully accurate.**

## conclusion

**In conclusion, the temperature change detection circuit described in this work uses a thermistor and LEDs to track temperature differences and offers a dependable and efficient solution. To clearly display temperature conditions, the circuit uses two LEDs: a Red LED (D1) and a Green LED (D2) also 3 Operational amplifiers in addition to different values of resistors and a temperature sensor which has 20K Thermistor.**

**If the temperature is within a specified range, the two LEDs will be off If the temperature increases above the upper limit, the Red LED D1 will glow If the temperature decreases below the lower limit, the Green LED D2 will glow.**

**Due to its ease of use and simplicity, this circuit is suitable for a range of applications.**